

ECEN 454


Lab 2

Roberto Luis


Section 505 - Rahul

Inverter:


Schematic:

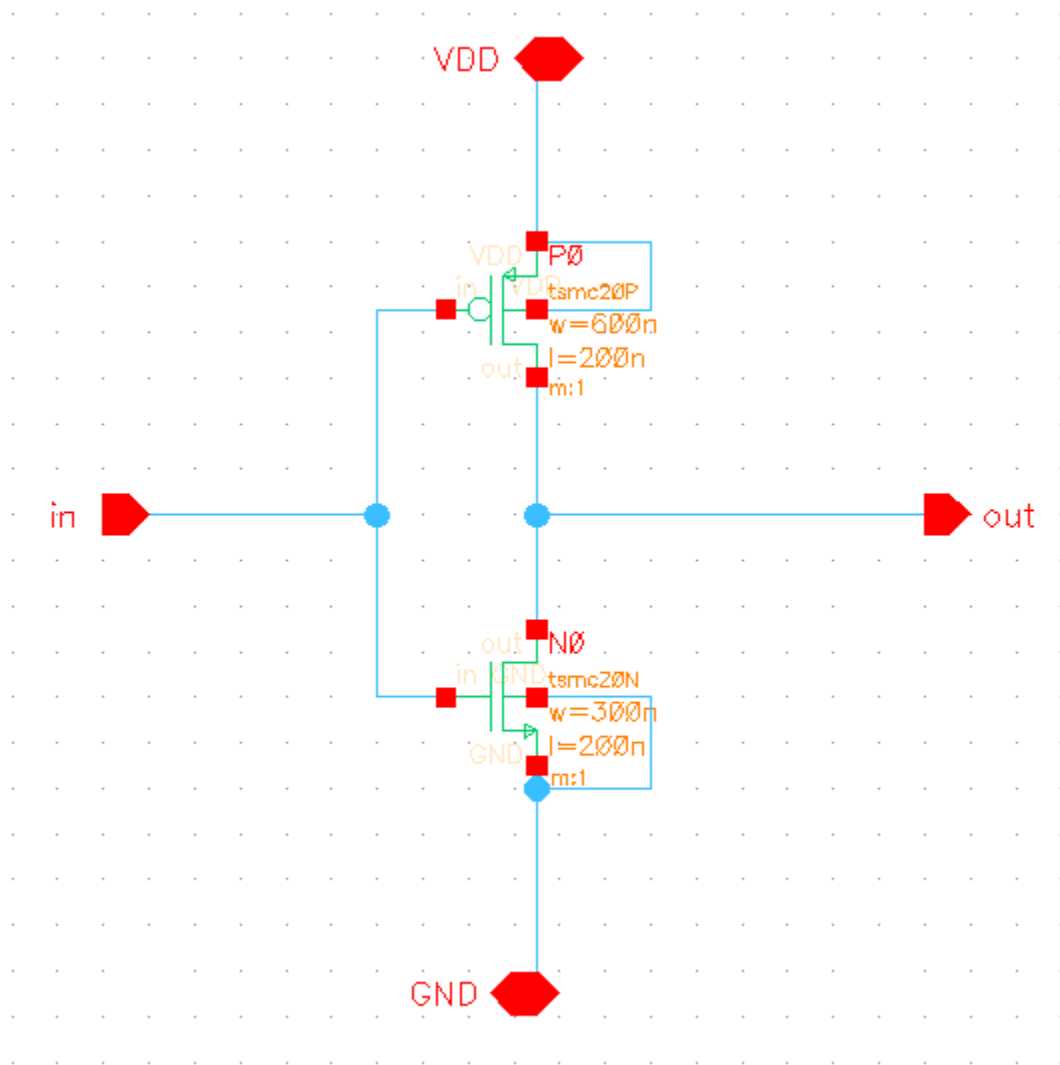


Symbol:

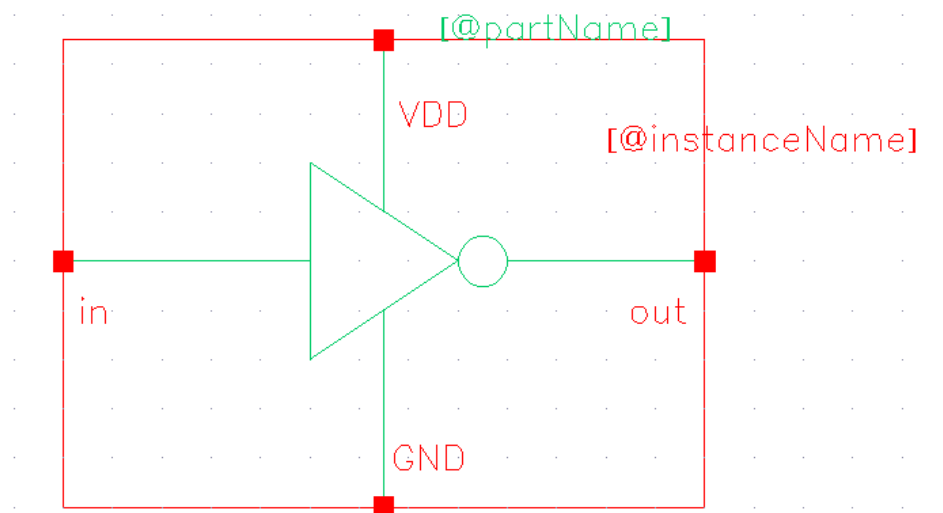

Layout:

 

Extracted:

 

LVS report:



The net-lists match.

	layout	schematic
instances		
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	2	2
total	2	2
nets		
un-matched	0	0
merged	0	0
pruned	0	0
active	4	4
total	4	4
terminals		
un-matched	0	0
matched but		
different type	0	0
total	4	4

Probe files from /home/ugrads/r/roberto.jluis/ecen454/LVS/schematic

devbad.out:

netbad.out:


mergenet.out:

termbad.out:


prunenet.out:

NAND:


Schematic:

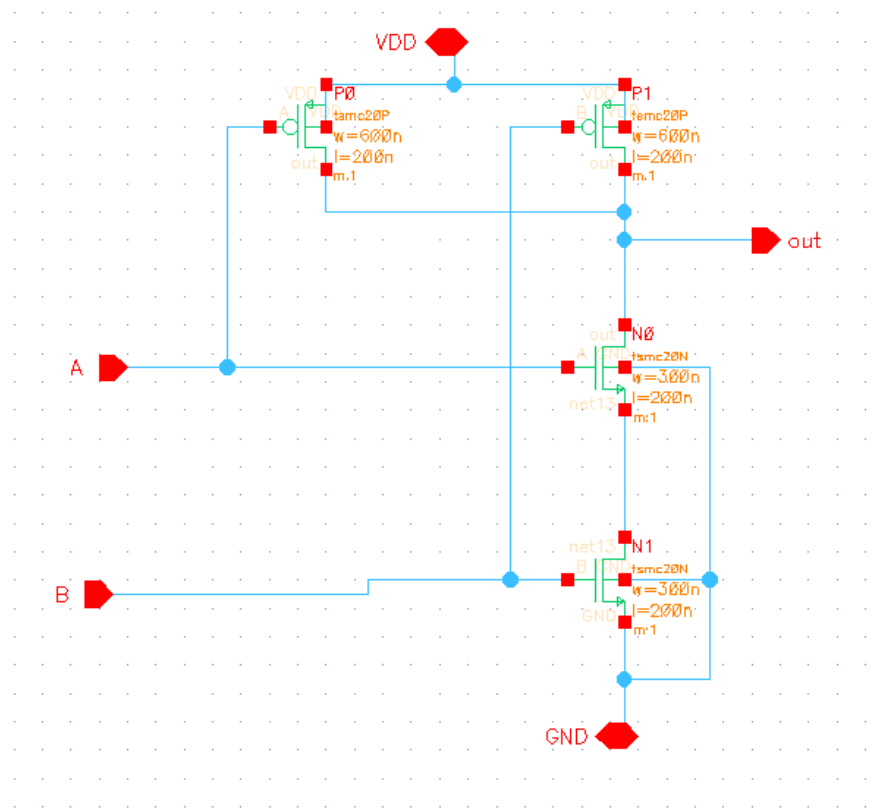


Symbol:

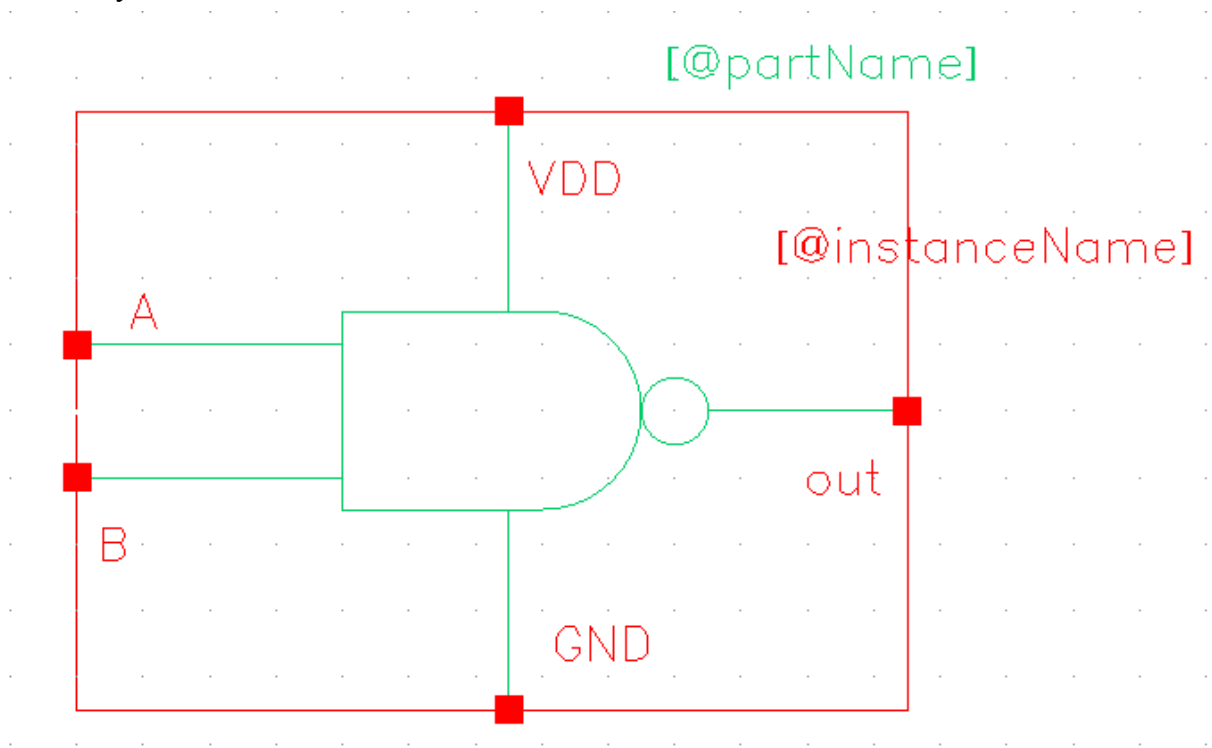

Layout:

 

Extracted:

 


LVS report:  
cap nret pret nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	4	4
total	4	4
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	6	6
total	6	6
	terminals	
un-matched	0	0
matched but different type	0	0
total	5	5

XOR:


Schematic:

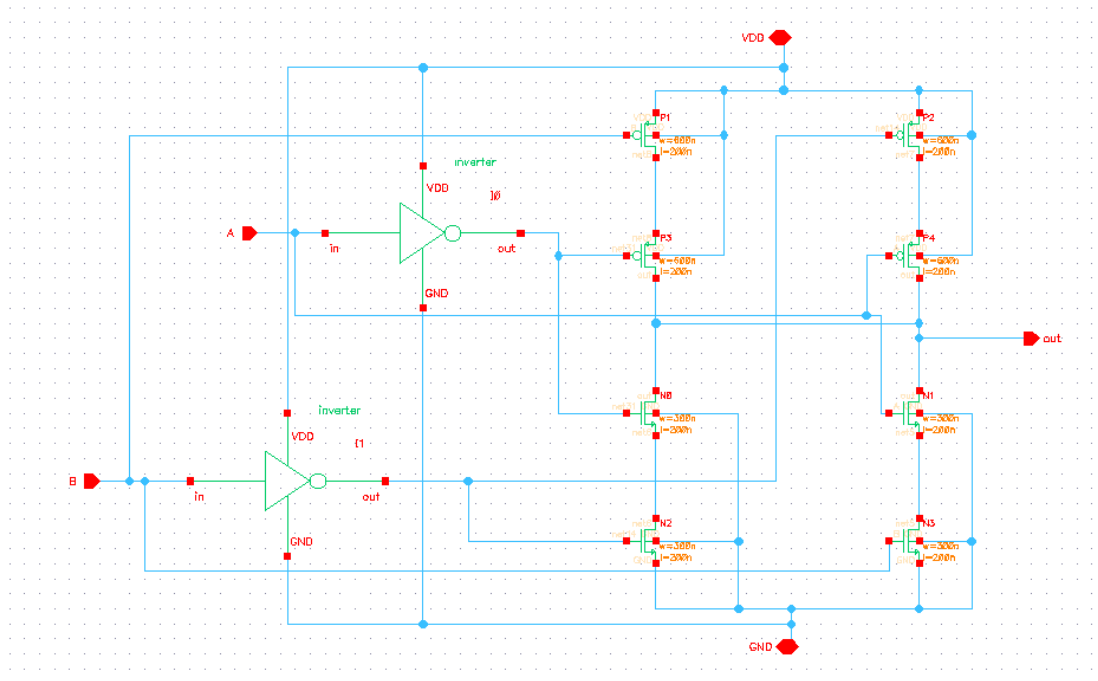

Symbol:

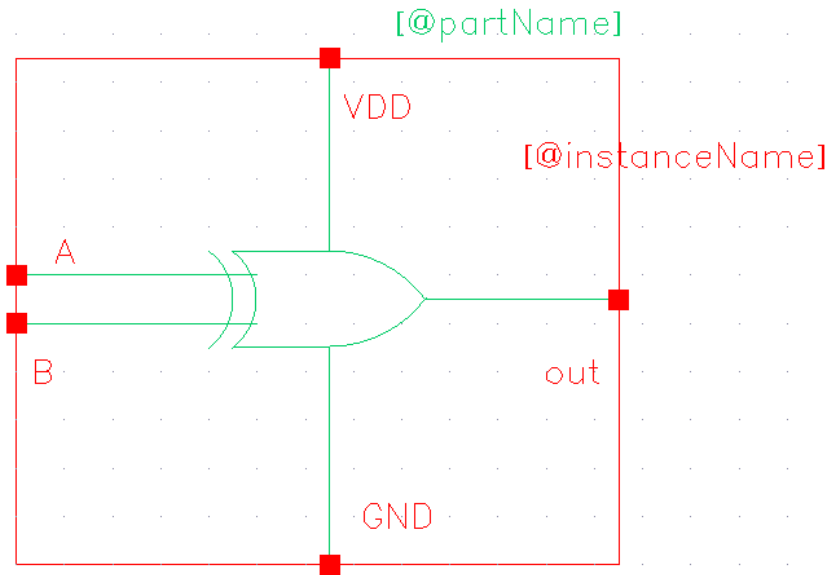


Layout:

 



Extracted:

 

LVS report:

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	12	12
total	12	12
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	11	11
total	11	11
	terminals	
un-matched	0	0
matched but different type	0	0
total	5	5

Note: The pins did not come out when I exported the image for the layouts but they are there.