
ECEN 454

Lab 5


Roberto Luis Section 505 - Rahul

Four-bit adder:


Schematic:

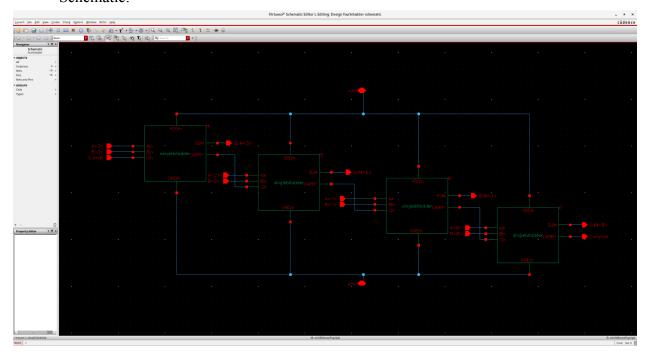


Layout:

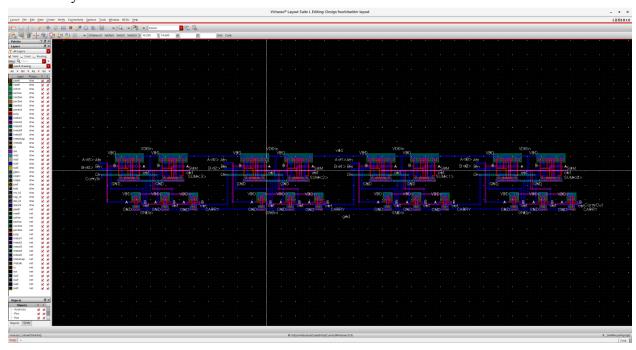


LVS report:

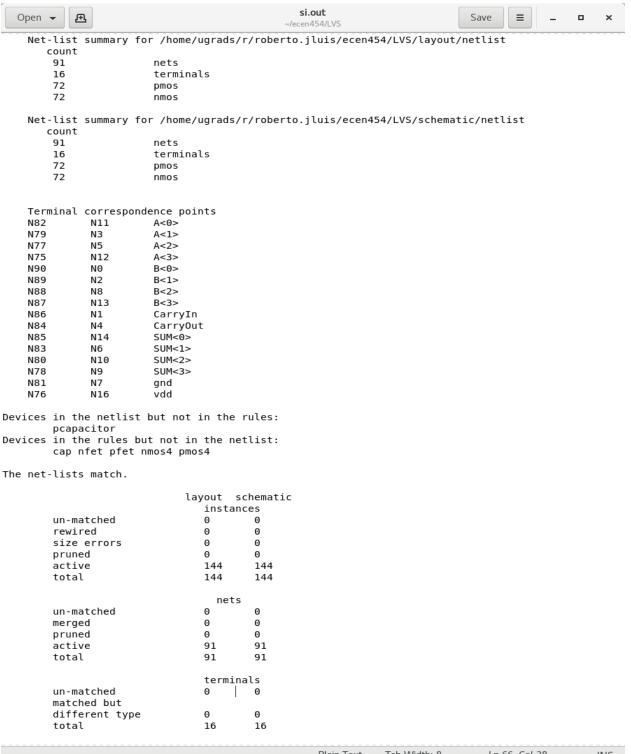


Test 1 waveform:

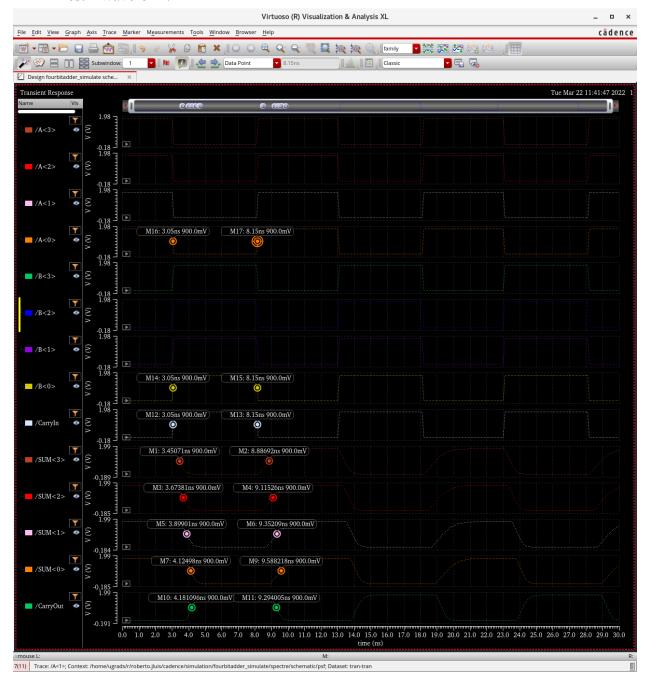


SUM<3>	.4 ns
SUM<2>	.62 ns
SUM<1>	.849 ns
SUM<0>	1.07 ns
CarryOut	1.13 ns

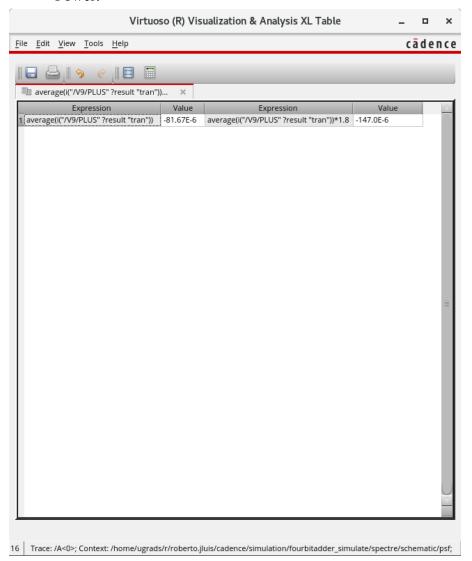


Test 2 waveform:

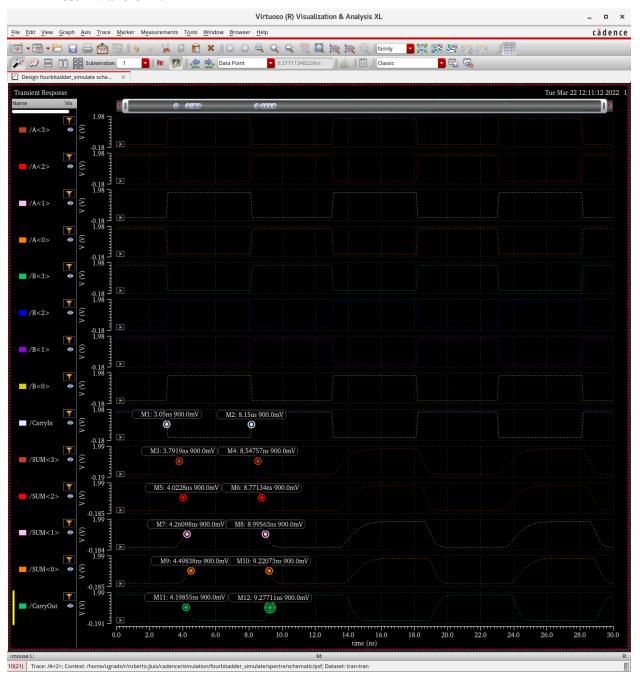


SUM<3>	.74 ns
SUM<2>	.97 ns
SUM<1>	1.21 ns
SUM<0>	1.448 ns
CarryOut	1.148 ns

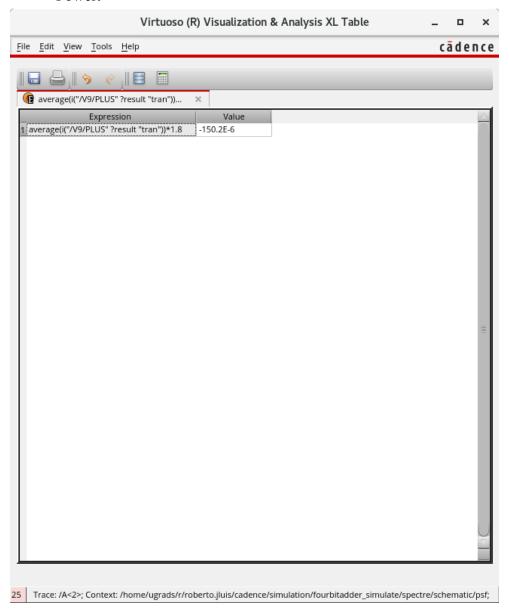


Test 3 waveform:

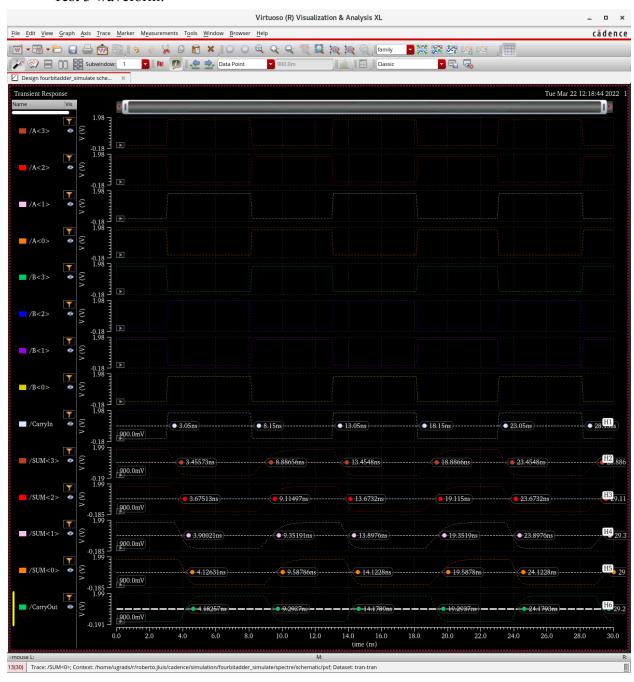

SUM<3>	.41 ns
SUM<2>	.625 ns
SUM<1>	.849 ns
SUM<0>	.85 ns
CarryOut	1.132 ns

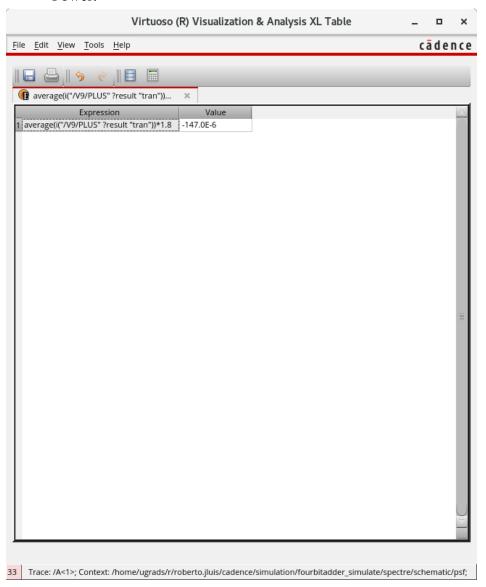

Test 4 waveform:

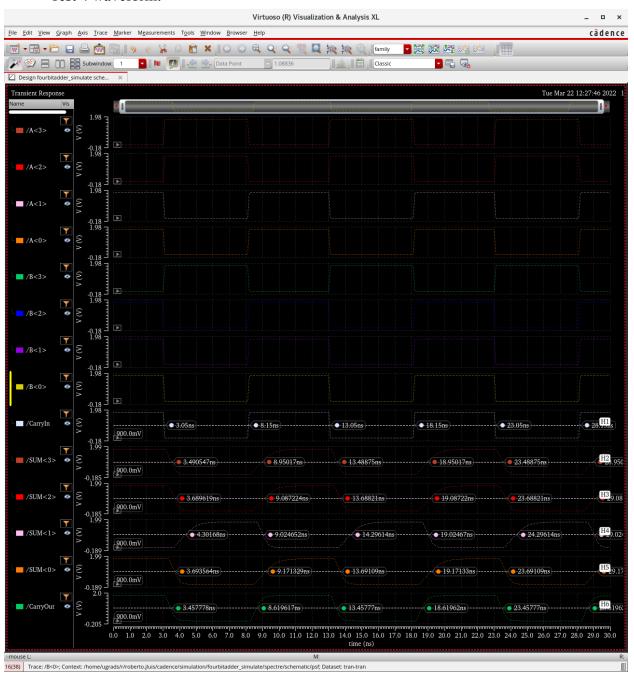

SUM<3>	.44 ns
SUM<2>	.639 ns
SUM<1>	1.251 ns
SUM<0>	.64 ns
CarryOut	.407 ns

